

For More Visit **VU Answer**

## CS302 Final Term Papers By Waqar (File 4)

Question No : 1 of 52	Marks: 1 (Budgeted Time 1 Min)
The hexadecimal value "FD" is equivalent to binary value _____	
Answer ( Please select your correct option )	
VuAnswers.com	
<input type="radio"/> 11011111	
<input type="radio"/> 11111101	correct
<input type="radio"/> 11001110	
<input type="radio"/> 00010111	
Made by: Waqar Siddhu	
Question No : 2 of 52	Marks: 1 (Budgeted Time 1 Min)
"A + B = B + A" is _____	
Answer ( Please select your correct option )	
VuAnswers.com	
<input type="radio"/> Demorgan's Law	
<input type="radio"/> Distributive Law	
<input type="radio"/> Commutative Law	correct
<input type="radio"/> Associative Law	
Made by: Waqar Siddhu	
Question No : 3 of 52	Marks: 1 (Budgeted Time 1 Min)
_____ is invalid number of cells in a single group formed by the adjacent cells in K-map	
Answer ( Please select your correct option )	
VuAnswers.com	
<input type="radio"/> 2	
<input type="radio"/> 8	
<input type="radio"/> 12	correct
<input type="radio"/> 16	
Made by: Waqar Siddhu	

For More Visit **VU Answer**

Question No : 4 of 52 Marks: 1 (Budgeted Time 1 Min)

The \_\_\_\_\_ Encoder is used as a keypad encoder.

Answer ( Please select your correct option ) **VuAnswers.com**

- 2-to-8 encoder
- 4-to-16 encoder
- BCD-to-Decimal
- Decimal-to-BCD Priority

**correct**     *Made by: Waqar Siddhu*

Question No : 5 of 52 Marks: 1 (Budgeted Time 1 Min)

The Programmable Array Logic (PAL) has \_\_\_\_\_ AND array and a \_\_\_\_\_ OR array

Answer ( Please select your correct option ) **VuAnswers.com**

- Fixed, programmable
- Programmable, fixed
- Fixed, fixed
- Programmable, programmable

**correct**     *Made by: Waqar Siddhu*

Question No : 6 of 52 Marks: 1 (Budgeted Time 1 Min)

74HC163 has two enable input pins which are \_\_\_\_\_ and \_\_\_\_\_.

Answer ( Please select your correct option ) **VuAnswers.com**

- ENP, ENT
- ENI, ENC
- ENP, ENC
- ENT, ENI

**correct**     *Made by: Waqar Siddhu*

# For More Visit **VU Answer**

Question No : 7 of 52 Marks: 1 (Budgeted Time 1 Min)

Given the state diagram of an up/down counter, we can find \_\_\_\_\_

Answer ( Please select your correct option ) **VuAnswers.com**

- The next state of a given present state
  - The previous state of a given present state
  - Both the next and previous states of a given state
  - The state diagram shows only the inputs/outputs of a given states
- Made by: Waqar Siddhu**

Question No : 8 of 52 Marks: 1 (Budgeted Time 1 Min)

A 4-bit parallel in / serial out shift register contains the value "0100", \_\_\_\_\_ clock signal(s) will be required to shift the value completely out of the register (i.e. to set the register to 0).

Answer ( Please select your correct option ) **VuAnswers.com**

- 1
  - 2
  - 3
  - 4
- Made by: Waqar Siddhu**

Question No : 9 of 52 Marks: 1 (Budgeted Time 1 Min)

In Single-Precision Floating Point format, "exponent" is represented by \_\_\_\_\_ bits.

Answer ( Please select your correct option ) **VuAnswers.com**

- 8-bits
  - 16-bits
  - 32-bits
  - 64-bits
- Made by: Waqar Siddhu**

# For More Visit **VU Answer**

Question No : 10 of 52 Marks: 1 (Budgeted Time 1 Min)

A particular Full Adder has \_\_\_\_\_ inputs and \_\_\_\_\_ output(s).

Answer ( Please select your correct option ) **VuAnswers.com**

- 2, 3
  - 2, 2
  - 3, 2 correct
  - 3, 3
- Made by: Waqar Siddhu**

Question No : 11 of 52 Marks: 1 (Budgeted Time 1 Min)

Programmable Array Logic (PAL) has \_\_\_\_\_ input(s) and \_\_\_\_\_ output(s).

Answer ( Please select your correct option ) **VuAnswers.com**

- Single, multiple
  - Multiple, single
  - Single, single
  - Multiple, multiple correct
- Made by: Waqar Siddhu**

Question No : 12 of 52 Marks: 1 (Budgeted Time 1 Min)

At  $S = 0$  and  $R = 1$ , an active-HIGH SR latch is in \_\_\_\_\_ condition.

Answer ( Please select your correct option ) **VuAnswers.com**

- SET
  - RESET correct not sure
  - Invalid
  - No change
- Made by: Waqar Siddhu**

For More Visit **VU Answer**

Question No : 13 of 52 Marks: 1 (Budgeted Time 1 Min)

At  $J = 1$ , and  $K = 1$ , output of JK Flip-flop will be \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

Set

Reset

Toggle

Invalid

correct

Made by: Waqar Siddhu

Question No : 14 of 52 Marks: 1 (Budgeted Time 1 Min)

The negative edge triggered flip-flop changes state on \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

Positive half cycle of clock

Negative half of clock

Low-to-high transition of clock

High-low transition of clock

correct

Made by: Waqar Siddhu

Question No : 15 of 52 Marks: 1 (Budgeted Time 1 Min)

When four 1's are taken as a group on a Karnaugh map, the number of variables eliminated from the output expression is/are \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

1

2

3

4

correct

Made by: Waqar Siddhu

For More Visit **VU Answer**

# For More Visit **VU Answer**

Question No : 16 of 52

Marks: 1 (Budgeted Time 1 Min)

The \_\_\_\_\_ output of first 74HC163 counter is connected to \_\_\_\_\_ and \_\_\_\_\_ inputs of other 74HC163 counter to form a single cascaded counter

Answer ( Please select your correct option )

**VuAnswers.com**

RCO, ENT, ENP

**correct**

ENT, RCO, ENP

ENP, RCO, ENT

RCO, ENI, ENC

**Made by: Waqar Siddhu**

Question No : 17 of 52

Marks: 1 (Budgeted Time 1 Min)

The design and implementation of synchronous counters start from \_\_\_\_\_

Answer ( Please select your correct option )

**VuAnswers.com**

Truth table

K-map

State table

State diagram

**correct**

**Made by: Waqar Siddhu**

Question No : 18 of 52

Marks: 1 (Budgeted Time 1 Min)

The best state assignment tends to \_\_\_\_\_

Answer ( Please select your correct option )

**VuAnswers.com**

Maximizes the number of state variables that don't change in a group of related states

**correct**

Minimizes the number of state variables that don't change in a group of related states

Minimizes the equivalent states

Maximizes the equivalent states

**Made by: Waqar Siddhu**

# For More Visit **VU Answer**

# For More Visit **VU Answer**

Question No : 19 of 52

Marks: 1 (Budgeted Time 1 Min)

In \_\_\_\_\_, the  $\bar{Q}$  output of the last flip-flop of the shift register is connected to the data input of the first flip-flop.

Answer ( Please select your correct option )

**VuAnswers.com**

- Moore machine
- Mealy machine
- Johnson counter
- Ring counter

correct

**Made by: Waqar Siddhu**

Question No : 20 of 52

Marks: 1 (Budgeted Time 1 Min)

In \_\_\_\_\_, the Q output of the last flip-flop of the shift register is connected to the data input of the first flip-flop of the shift register.

Answer ( Please select your correct option )

**VuAnswers.com**

- Moore machine
- Mealy machine
- Johnson counter
- Ring counter

correct

**Made by: Waqar Siddhu**

Question No : 21 of 52

Marks: 1 (Budgeted Time 1 Min)

If  $S=1$  and  $R=0$ , then  $Q(t+1) =$  \_\_\_\_\_ for positive edge triggered flip-flop

Answer ( Please select your correct option )

**VuAnswers.com**

- 0
- 1
- Invalid
- Input is invalid

correct

**Made by: Waqar Siddhu**

# For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 22 of 52 Marks: 1 (Budgeted Time 1 Min)

For a gated D-Latch, if EN=1 and D=1 then  $Q(t+1) =$  \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

- 0
- 1
- $Q(t)$
- Invalid

Made by: Waqar Siddhu

Question No : 23 of 52 Marks: 1 (Budgeted Time 1 Min)

Which of the following is NOT a sequential circuit?

Answer ( Please select your correct option )

VuAnswers.com

- SR latch
- Counter
- Full Adder
- JK Flip-flop

correct

Made by: Waqar Siddhu

Question No : 24 of 52 Marks: 1 (Budgeted Time 1 Min)

Each stage of Master-slave flip-flop works in \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

- One complete clock signal
- One fourth of the clock signal
- One third of the clock signal
- One half of the clock signal

correct Made by: Waqar Siddhu

For More Visit **VU Answer**



# For More Visit **VU Answer**

Question No : 25 of 52

Marks: 1 (Budgeted Time 1 Min)

The counter states can be determined by the formula: \_\_\_\_\_ ("n" represents the total number of flip-flops).

Answer ( Please select your correct option )

VuAnswers.com

- $n^2$  (n raise to power 2)
- $n^2-1$  (n raise to power 2 and then minus 1)
- $2^n$  (2 raise to power n)
- $2^n-1$  (2 raise to power n and then minus 1)

correct

Made by: Waqar Siddhu

Question No : 26 of 52

Marks: 1 (Budgeted Time 1 Min)

RCO Stands for \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

- Reconfiguration Counter Output
- Reconfiguration Clock Output
- Ripple Counter Output
- Ripple Clock Output

correct Made by: Waqar Siddhu

Question No : 27 of 52

Marks: 1 (Budgeted Time 1 Min)

A divide-by-50 counter divides the input \_\_\_\_\_ signal to a 1 Hz signal.

Answer ( Please select your correct option )

VuAnswers.com

- 10 Hz
- 50 Hz
- 100 Hz
- 500 Hz

correct

Made by: Waqar Siddhu

# For More Visit **VU Answer**

Question No : 28 of 52 Marks: 1 (Budgeted Time 1 Min)

The alternate solution for a demultiplexer-register combination circuit is \_\_\_\_\_

Answer ( Please select your correct option ) **VuAnswers.com**

- Parallel in / Serial out shift register
  - Serial in / Parallel out shift register
  - Parallel in / Parallel out shift register
  - Serial in / Serial Out shift register
- correct**
- Made by: Waqar Siddhu**

Question No : 29 of 52 Marks: 1 (Budgeted Time 1 Min)


In asynchronous transmission when the transmission line is idle, \_\_\_\_\_

Answer ( Please select your correct option ) **VuAnswers.com**

- It is set to logic low
  - It is set to logic high
  - Remains in previous state
  - State of transmission line is not used to start transmission
- correct**
- Made by: Waqar Siddhu**

 Question No : 30 of 52 Marks: 1 (Budgeted Time 1 Min)

The output of this circuit is always \_\_\_\_\_



Answer ( Please select your correct option ) **VuAnswers.com**

- 1
  - 0
  - A
  - $\bar{A}$
- correct**
- Made by: Waqar Siddhu**

Question No : 31 of 52 Marks: 1 (Budgeted Time 1 Min)

Which is not characteristic of a shift register?

Answer ( Please select your correct option ) **VuAnswers.com**

- Serial in/parallel in
  - Serial in/parallel out
  - Parallel in/serial out
  - Parallel in/parallel out
- correct**
- Made by: Waqar Siddhu**

Question No : 32 of 52 Marks: 1 (Budgeted Time 1 Min)

A Nibble consists of \_\_\_\_ bits

Answer ( Please select your correct option ) **VuAnswers.com**

- 2
  - 4
  - 8
  - 16
- correct**
- Made by: Waqar Siddhu**

Question No : 33 of 52 Marks: 1 (Budgeted Time 1 Min)

The \_\_\_\_\_ of a ROM is the time it takes for the data to appear at the Data Output of the ROM chip after an address is applied at the address input lines

Answer ( Please select your correct option ) **VuAnswers.com**

- Write Time
  - Refresh Time
  - Refresh Time
  - Access Time
- correct**
- Made by: Waqar Siddhu**

Question No : 34 of 52

Marks: 1 (Budgeted Time 1 Min)

In \_\_\_\_\_, all the columns in the same row are either read or written.

Answer ( Please select your correct option )

VuAnswers.com

- Sequential Access
- MOS Access
- FAST Mode Page Access
- None of given options

correct

Made by: Waqar Siddhu

Question No : 35 of 52

Marks: 1 (Budgeted Time 1 Min)

In order to synchronize two devices that consume and produce data at different rates, we can use \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

- Read Only Memory
- First In First Out Memory
- Flash Memory
- Fast Page Access Mode Memory

correct

Made by: Waqar Siddhu

Question No : 36 of 52

Marks: 1 (Budgeted Time 1 Min)

The process of converting the analogue signal into a digital representation (code) is known as \_\_\_\_\_

Answer ( Please select your correct option )

VuAnswers.com

- Strobing
- Amplification
- Quantization
- Digitization

correct

Made by: Waqar Siddhu

Question No : 37 of 52 Marks: 1 (Budgeted Time 1 Min)

A hold action occurs :

Answer ( Please select your correct option ) **VuAnswers.com**

- After the analog-to-digital conversion
  - During each sample
  - Immediately after a sample
  - Before each sample
- Made by: Waqar Siddhu**

Question No : 38 of 52 Marks: 1 (Budgeted Time 1 Min)

A flash A/D converter uses :

Answer ( Please select your correct option ) **VuAnswers.com**

- Counters
  - Flip-flops
  - Op-amps correct
  - An integrator
- Made by: Waqar Siddhu**

Question No : 39 of 52 Marks: 1 (Budgeted Time 1 Min)

\_\_\_\_\_ of a D/A converter is determined by comparing the actual output of a D/A converter with the expected output.

Answer ( Please select your correct option ) **VuAnswers.com**

- Resolution
  - Accuracy correct
  - Quantization
  - Missing Code
- Made by: Waqar Siddhu**

Question No : 40 of 52 Marks: 1 (Budgeted Time 1 Min)

Sampling of an analog signal produces :

Answer ( Please select your correct option ) **VuAnswers.com**

- A series of impulses those are proportional to the frequency of the signal
  - A series of impulses those are proportional to the amplitude of the signal
  - Digital codes that represent the analog signal amplitude
  - Digital codes that represent the time of each sample
- Made by: Waqar Siddhu**

Question No : 41 of 52 Marks: 2 (Budgeted Time 4 Min)

How many 4-bit Parallel Adders are required to add two BCD digits?

Answer ( Please [click here](#) to Add Answer ) **VuAnswers.com**

Rich text editor toolbar with options: Normal, Arial, 12, Bold, Italic, Underline, Bulleted List, Numbered List, Indent, Outdent, Undo, Redo, 100%.

**Made by: Waqar Siddhu**

Question No : 42 of 52 Marks: 2 (Budgeted Time 4 Min)

What is meant by "excitation inputs"?

Answer ( Please [click here](#) to Add Answer ) **VuAnswers.com**

Rich text editor toolbar with options: Normal, Arial, 12, Bold, Italic, Underline, Bulleted List, Numbered List, Indent, Outdent, Undo, Redo, 100%.

**Made by: Waqar Siddhu**

For More Visit **VU Answer**

Question No : 43 of 52

Marks: 2 (Budgeted Time 4 Min)

How many bytes will be there in  $32\text{ K} \times 4$  memory?

Answer ( Please [click here](#) to Add Answer )

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 44 of 52

Marks: 2 (Budgeted Time 4 Min)

Generally two types of D/A Converters are used. Write down their names.

Answer ( Please [click here](#) to Add Answer )

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 45 of 52

Marks: 3 (Budgeted Time 6 Min)

Draw the function table of an Half adder circuit.

Answer ( Please [click here](#) to Add Answer )

VuAnswers.com

Normal Arial 12 B I U


Made by: Waqar Siddhu

For More Visit **VU Answer**

# For More Visit **VU Answer**

 
Question No : 46 of 52 Marks: 3 (Budgeted Time 6 Min)

Following is an incomplete diagram. Name the gate which can be placed in red boxes A and B to configure 74HC161 as a Mod-9 counter.



Answer ( Please [click here](#) to Add Answer )

**VuAnswers.com**

 

*Made by: Waqar Siddhu*


Question No : 47 of 52 Marks: 3 (Budgeted Time 6 Min)

Draw a circuit diagram of flip-flop based static memory cell.



Answer ( Please [click here](#) to Add Answer )

**VuAnswers.com**

 

*Made by: Waqar Siddhu*

Question No : 48 of 52 Marks: 3 (Budgeted Time 6 Min)

What is RAM Stack, which register stores the address of top of the stack?



Answer ( Please [click here](#) to Add Answer )

**VuAnswers.com**



*Made by: Waqar Siddhu*

# For More Visit **VU Answer**



For More Visit **VU Answer**

Question No : 49 of 52

Marks: 5 (Budgeted Time 10 Min)

Simplify the following Boolean expression so that it uses minimum number of gates.

$$\overline{(A+B+C+D)} + \overline{(ABC)}$$

Answer ( Please [click here](#) to Add Answer )

**VuAnswers.com**




*Made by: Waqar Siddhu*

 Question No : 50 of 52

Marks: 5 (Budgeted Time 10 Min)

You are given the block diagram of 74HC163 4-bit Synchronous Counter. Connect two 74HC163 4-bit Synchronous Counters to form a single Cascaded Decade Counter.



Answer ( Please [click here](#) to Add Answer )

**VuAnswers.com**



*Made by: Waqar Siddhu*

For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 51 of 52


Marks: 5 (Budgeted Time 10 Min)

State table for a mealy machine is given below. Derive a state diagram for mealy machine from this state table.

Present State	Next State				Output Z			
	XY 00	XY 01	XY 10	XY 11	XY 00	XY 01	XY 10	XY 11
A	A	C	B	C	0	1	0	1
B	B	D	C	D	0	0	0	0

Answer ( Please [click here](#) to Add Answer )

VuAnswers.com



*Made by: Waqar Siddhu*

Question No : 52 of 52

Marks: 5 (Budgeted Time 10 Min)

What is operational amplifier and how it can be used as an inverting amplifier? Write down the relation for its voltage gain.

Answer ( Please [click here](#) to Add Answer )

VuAnswers.com



*Made by: Waqar Siddhu*

For More Visit **VU Answer**