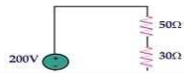


Question No : 1 of 26		Marks: 1 (Budgeted Time 1 Min)
<p>Which battery applies a greater potential difference?</p>		
Answer ( Please select your correct option )		
<input type="radio"/>	12v	
<input type="radio"/>	1.5v	
<input type="radio"/>	10v	
<input type="radio"/>	0.5v	
Made By: Waqar Siddhu		
Question No : 2 of 26		Marks: 1 (Budgeted Time 1 Min)
<p>If we connect n inductances in parallel the combined effect of all these inductances is</p>		
Answer ( Please select your correct option )		
<input type="radio"/>	equal to the sum of individual inductance.	
<input type="radio"/>	reciprocal of combined effect of all these inductances	
<input type="radio"/>	product of all	
<input type="radio"/>	sum of first and last	
Made By: Waqar Siddhu		
Question No : 3 of 26		Marks: 1 (Budgeted Time 1 Min)
<p>Voltage is measured in</p>		
Answer ( Please select your correct option )		
<input type="radio"/>	ohm	
<input type="radio"/>	farad	
<input type="radio"/>	volt	
<input type="radio"/>	power	
Made By: Waqar Siddhu		

Question No : 4 of 26

Marks: 1 (Budgeted Time 1 Min)

Through which resistance least current will flow




Answer ( Please select your correct option )

- ☐ 50Ω
- ☐ 30Ω
- ☐ 20Ω
- ☐ same through all resistance

**Made By: Waqar Siddhu**

Question No : 4 of 26

Marks: 1 (Budgeted Time 1 Min)

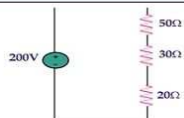

Answer ( Please select your correct option )

- ☐ 50Ω
- ☐ 30Ω
- ☐ 20Ω
- ☐ same through all resistance

**Made By: Waqar Siddhu**

Question No : 5 of 26

Marks: 1 (Budgeted Time 1 Min)

Resistance of an open circuit is

- ☐ Moderate
- ☐ Infinitely high
- ☐ Low
- ☐ Zero

**Made By: Waqar Siddhu**

Question No : 6 of 26

Marks: 1 (Budgeted Time 1 Min)

When two resistances are connected in series

Answer ( Please select your correct option )

- ☐ They must both have same resistance value.
- ☐ The voltage across each must be the same.
- ☐ They must have different resistance value.
- ☐ There is only one path for current for both resistances

**Made By: Waqar Siddhu**

Question No : 7 of 26

Marks: 1 (Budgeted Time 1 Min)

If  $R_1$  and  $R_2$  resistances are connected in series and  $V_s$  is source voltage , then voltage drop across  $R_1$  can be calculated by which of the following formula.


Answer ( Please select your correct option )

- ☐  $V_1 = R_1 \times V_s / R_1 + R_2$
- ☐  $V_1 = R_2 \times V_s / R_1 + R_2$
- ☐  $V_1 = R_1 \times R_2 / V_s$
- ☐  $V_1 = R_1 \times V_s / R_1$

**Made By: Waqar Siddhu**

Question No : 8 of 26

Marks: 1 (Budgeted Time 1 Min)

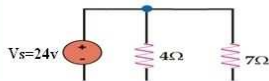For the given circuit, Voltage drop across  $4\Omega$  resistance is


Answer ( Please select your correct option )

- ☐ 6v
- ☐ 24v
- ☐ 8.72v
- ☐ 15.27v

**Made By: Waqar Siddhu**

Question No : 8 of 26

Marks: 1 (Budgeted Time 1 Min)

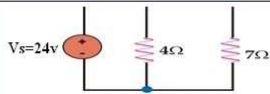

Answer ( Please select your correct option )


- ☐ 6v
- ☐ 24v
- ☐ 8.72v
- ☐ 15.27v

**Made By: Waqar Siddhu**

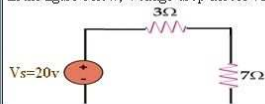Question No : 9 of 26

Marks: 1 (Budgeted Time 1 Min)

In the figure below, Voltage drop across 7Ω will be



Answer ( Please select your correct option )

- ☐ 20v
- ☐ 14v
- ☐ 6v
- ☐ 10v

**Made By: Waqar Siddhu**

Question No : 9 of 26

Marks: 1 (Budgeted Time 1 Min)




Answer ( Please select your correct option )

- ☐ 20v
- ☐ 14v
- ☐ 6v
- ☐ 10v

**Made By: Waqar Siddhu**

Question No : 10 of 26

Marks: 1 (Budgeted Time 1 Min)

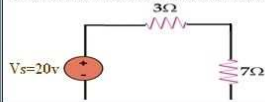Using voltage divider in the figure below, Voltage drop across  $3\Omega$  will be

Answer ( Please select your correct option )

C 20v

C 14v


C 6v

C 7v

**Made By: Waqar Siddhu**

Question No : 10 of 26

Marks: 1 (Budgeted Time 1 Min)

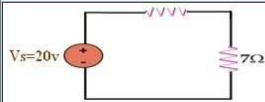

Answer ( Please select your correct option )

C 20v

C 14v

C 6v


C 7v

**Made By: Waqar Siddhu**

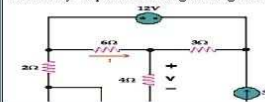Question No : 11 of 26

Marks: 1 (Budgeted Time 1 Min)

How many loops can be assigned to given figure?



Answer ( Please select your correct option )

C 2

C 4


C 3

C 5

**Made By: Waqar Siddhu**

Question No : 11 of 26

Marks: 1 (Budgeted Time 1 Min)

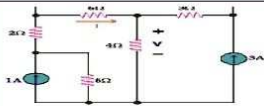

Answer ( Please select your correct option )


- ☐ 2
- ☐ 4
- ☐ 3
- ☐ 5

**Made By: Waqar Siddhu**

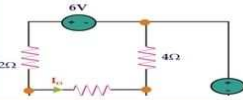Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)

The value of  $I_a$  for given circuit is




Answer ( Please select your correct option )

- ☐  $I_a = I_o$
- ☐  $I_a = 3A$
- ☐  $I_a = -3A$
- ☐  $I_a = 6V$

**Made By: Waqar Siddhu**

Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)

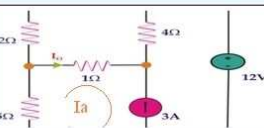

Answer ( Please select your correct option )

- ☐  $I_a = I_o$
- ☐  $I_a = 3A$
- ☐  $I_a = -3A$
- ☐  $I_a = 6V$

**Made By: Waqar Siddhu**

Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)



Answer ( Please select your correct option )

☐  $I_a = I_0$

☐  $I_a = 3A$

☐  $I_a = -3A$

☐  $I_a = 6V$

**Made By: Waqar Siddhu**

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

If value of  $I$  is  $2.2mA$ , what will be the value of  $I_0$ ?



Answer ( Please select your correct option )

☐  $2mA$

☐  $1mA$

☐  $2.2mA$

☐  $10mA$

**Made By: Waqar Siddhu**

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)



Answer ( Please select your correct option )

☐  $2mA$

☐  $1mA$

☐  $2.2mA$


☐  $10mA$

**Made By: Waqar Siddhu**

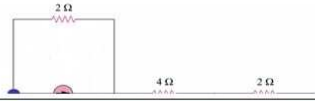Question No : 14 of 26

Marks: 1 (Budgeted Time 1 Min)

How many loop equations can be written for this circuit?




Answer ( Please select your correct option )

- ☐ 2
- ☐ 4
- ☐ 3
- ☐ 5

**Made By: Waqar Siddhu**

Question No : 14 of 26

Marks: 1 (Budgeted Time 1 Min)

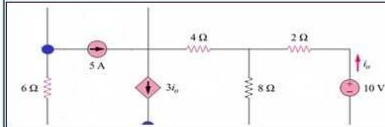


Answer ( Please select your correct option )

- ☐ 2
- ☐ 4
- ☐ 3
- ☐ 5

**Made By: Waqar Siddhu**

Question No : 14 of 26

Marks: 1 (Budgeted Time 1 Min)

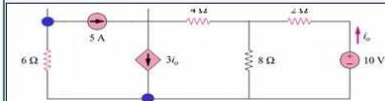

Answer ( Please select your correct option )

- ☐ 2
- ☐ 4
- ☐ 3
- ☐ 5


**Made By: Waqar Siddhu**



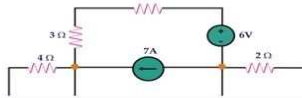Question No : 15 of 26

Marks: 1 (Budgeted Time 1 Min)

For the given diagram, value of coupling equation may be




Answer ( Please select your correct option )

☐  $V_1 - V_2 = 6V$ 
☐  $V_1 - V_2 = 2V$ 
☐  $I_1 - I_2 = 7A$ 
☐  $V_1 - V_2 = 7V$ 
**Made By: Waqar Siddhu**

Question No : 15 of 26

Marks: 1 (Budgeted Time 1 Min)

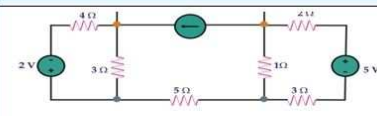

Answer ( Please select your correct option )

☐  $V_1 - V_2 = 6V$ 
☐  $V_1 - V_2 = 2V$ 
☐  $I_1 - I_2 = 7A$ 
☐  $V_1 - V_2 = 7V$ 
**Made By: Waqar Siddhu**

Question No : 16 of 26

Marks: 1 (Budgeted Time 1 Min)

The algebraic sum of the voltages around any loop is zero, is statement of

☐ Kirchhof, s voltage law


☐ Kirchhof, s current law

☐ Ohm, s law

☐ Farady law
**Made By: Waqar Siddhu**

Question No : 17 of 26

Marks: 1 (Budgeted Time 1 Min)

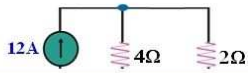
Using current divider rule, current flowing through  $4\Omega$  is

Answer ( Please select your correct option )

☐ 4A☐ 8A☐ 12A☐ 3A**Made By: Waqar Siddhu**

Question No : 17 of 26

Marks: 1 (Budgeted Time 1 Min)

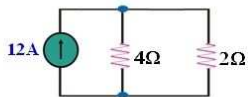


Answer ( Please select your correct option )

☐ 4A☐ 8A☐ 12A☐ 3A**Made By: Waqar Siddhu**

Question No : 18 of 26

Marks: 1 (Budgeted Time 1 Min)

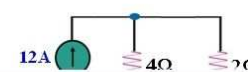
In the fig. below current flowing through  $2\Omega$  is

Answer ( Please select your correct option )

☐ 4A☐ 8A☐ 12A☐ 6A**Made By: Waqar Siddhu**

Question No : 18 of 26

Marks: 1 (Budgeted Time 1 Min)

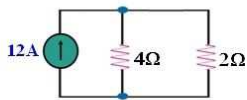

Answer ( Please select your correct option )


- ☐ 4A
- ☐ 8A
- ☐ 12A
- ☐ 6A

**Made By: Waqar Siddhu**

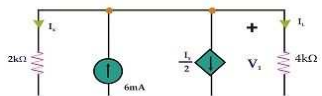Question No : 19 of 26

Marks: 1 (Budgeted Time 1 Min)

In the given circuit, the value of independent current source is




Answer ( Please select your correct option )

- ☐  $I_x$
- ☐  $I_x/2$
- ☐ 6mA
- ☐  $I_L$

**Made By: Waqar Siddhu**

Question No : 19 of 26

Marks: 1 (Budgeted Time 1 Min)

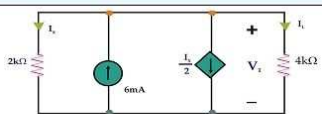

Answer ( Please select your correct option )


- ☐  $I_x$
- ☐  $I_x/2$
- ☐ 6mA
- ☐  $I_L$

**Made By: Waqar Siddhu**

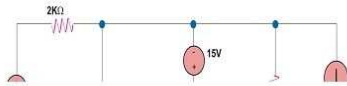Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

How many loop/mesh equations we can write for the given circuit?




Answer ( Please select your correct option )

- ☐ 3
- ☐ 4
- ☐ 5
- ☐ 1

**Made By: Waqar Siddhu**

Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

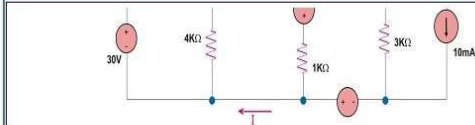


Answer ( Please select your correct option )

- ☐ 3
- ☐ 4
- ☐ 5
- ☐ 1

**Made By: Waqar Siddhu**

Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

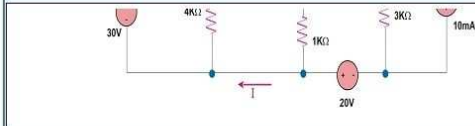

Answer ( Please select your correct option )


- ☐ 3
- ☐ 4
- ☐ 5
- ☐ 1

**Made By: Waqar Siddhu**

Question No : 21 of 26

Marks: 2 (Budgeted Time 4 Min)

Just write KVL equation for mesh 1

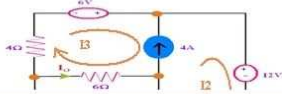


Answer ( Please click here to Add Answer )

Rich text editor toolbar with options: Normal, Arial, 12, Bold, Italic, Underline, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

Question No : 21 of 26

Marks: 2 (Budgeted Time 4 Min)

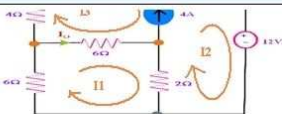

Answer ( Please click here to Add Answer )


Rich text editor toolbar with options: Normal, Arial, 12, Bold, Italic, Underline, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

Question No : 22 of 26

Marks: 2 (Budgeted Time 4 Min)

Calculate Voltage  $V_{AB}$

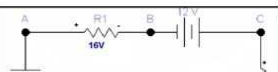


Answer ( Please click here to Add Answer )

Rich text editor toolbar with options: Normal, Arial, 12, Bold, Italic, Underline, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

Question No : 22 of 26

Marks: 2 (Budgeted Time 4 Min)

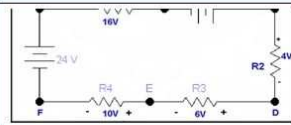

Answer ( Please click here to Add Answer )


Rich text editor toolbar with options: Bold, Italic, Underline, Text Color, Background Color, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

Question No : 23 of 26

Marks: 3 (Budgeted Time 6 Min)

Write KVL equation for super mesh.

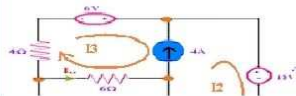


Answer ( Please click here to Add Answer )

Rich text editor toolbar with options: Bold, Italic, Underline, Text Color, Background Color, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

Question No : 23 of 26

Marks: 3 (Budgeted Time 6 Min)

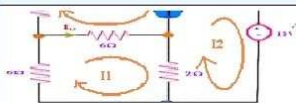

Answer ( Please click here to Add Answer )


Rich text editor toolbar with options: Bold, Italic, Underline, Text Color, Background Color, Bulleted List, Numbered List, Indent, Outdent, Link, Unlink, Image, Table, Undo, Redo, and a 100% zoom level.

**Made By: Waqar Siddhu**

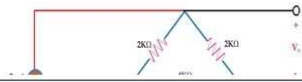Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

Just label the diagram by any method and mention the value of source current in the circuit.




Answer ( [Please click here to Add Answer](#) )

Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

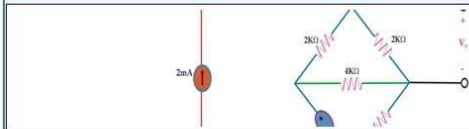


Answer ( [Please click here to Add Answer](#) )

Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

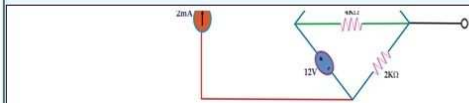

Answer ( [Please click here to Add Answer](#) )


Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 25 of 26

Marks: 5 (Budgeted Time 10 Min)

Identify and label each mesh otherwise you will lose your marks. Label circuit diagram properly. Write KVL equation for super mesh.

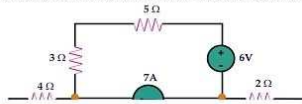
Answer ( [Please click here to Add Answer](#) )

Rich text editor toolbar with options for font style (Normal, Arial), size (12), bold, italic, underline, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 25 of 26

Marks: 5 (Budgeted Time 10 Min)

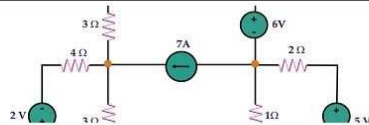
Answer ( [Please click here to Add Answer](#) )

Rich text editor toolbar with options for font style (Normal, Arial), size (12), bold, italic, underline, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 25 of 26

Marks: 5 (Budgeted Time 10 Min)

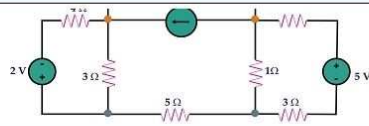Answer ( [Please click here to Add Answer](#) )

Rich text editor toolbar with options for font style (Normal, Arial), size (12), bold, italic, underline, and alignment. The text area is empty.


**Made By: Waqar Siddhu**



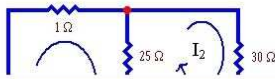Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

For given figure, write KVL equation for Mesh 1 and 2.




Answer ( Please click here to Add Answer )

Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

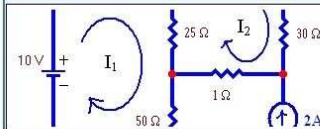


Answer ( Please click here to Add Answer )

Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**

Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

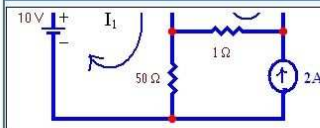

Answer ( Please click here to Add Answer )

Rich text editor toolbar with options for font style, size, color, and alignment. The text area is empty.

**Made By: Waqar Siddhu**