

Question No : 4 of 52 Marks: 1 (Budgeted Time 1 Min)

$A + \bar{A}B =$ _____

Answer (Please select your correct option)

VuAnswers.com

- A
- B
- A.B
- A+B

correct

Made by: Waqar Siddhu

Question No : 5 of 52 Marks: 1 (Budgeted Time 1 Min)

$\bar{A}B + \bar{A}B\bar{C} + AC$ is an example of _____

Answer (Please select your correct option)

VuAnswers.com

- Product of sum form
- Sum of product form
- Demorgans law
- Associative law

correct

Made by: Waqar Siddhu

Question No : 6 of 52 Marks: 1 (Budgeted Time 1 Min)

A standard POS form has _____ terms that have all the variables in the domain of the expression.

Answer (Please select your correct option)

VuAnswers.com

- Sum
- Product
- Min
- Composite

correct

Made by: Waqar Siddhu

Question No : 7 of 52 Marks: 1 (Budgeted Time 1 Min)

74HC163 has two enable input pins which are _____ and _____.

Answer (Please select your correct option) **VuAnswers.com**

- ENP, ENT correct
 - ENI, ENC
 - ENP, ENC
 - ENT, ENI
- Made by: Waqar Siddhu**

Question No : 8 of 52 Marks: 1 (Budgeted Time 1 Min)

Given the state diagram of an up/down counter, we can find _____.

Answer (Please select your correct option) **VuAnswers.com**

- The next state of a given present state correct
 - The previous state of a given present state
 - Both the next and previous states of a given state
 - The state diagram shows only the inputs/outputs of a given states
- Made by: Waqar Siddhu**

Question No : 9 of 52 Marks: 1 (Budgeted Time 1 Min)

A multiplexer with a register circuit converts _____.

Answer (Please select your correct option) **VuAnswers.com**

- Serial data to parallel
 - Parallel data to serial correct
 - Serial data to serial
 - Parallel data to parallel
- Made by: Waqar Siddhu**

Question No : 10 of 52 Marks: 1 (Budgeted Time 1 Min)

What will be output state when $J = 1$, $K = 0$ and CLR input is active?

Answer (Please select your correct option)

VuAnswers.com

Q = 1

correct

Q = 0

Retains previous output state

Toggle output

Made by: Waqar Siddhu

Question No : 11 of 52 Marks: 1 (Budgeted Time 1 Min)

When $PRE' = 0$ and $CLR' = 1$, $Q_t = 0$ then $Q_{(t+1)}$ will be _____

Answer (Please select your correct option)

VuAnswers.com

Output of flip-flop will be set (Logic 1)

correct

Output of flip-flop will be reset (Logic 0)

Output of flip-flop will be invalid

Flip-flop will change output on Clock transition

Made by: Waqar Siddhu

Question No : 12 of 52 Marks: 1 (Budgeted Time 1 Min)

Compared to analog systems, digital systems _____.

Answer (Please select your correct option)

VuAnswers.com

are less prone to noise

correct

not sure

can represent an infinite number of values

can handle much higher power

occupy large space

Made by: Waqar Siddhu

For More Visit **VU Answer**

Question No : 13 of 52

Marks: 1 (Budgeted Time 1 Min)

When one 1 is taken as a group on a Karnaugh map, the number of variables eliminated from the output expression is/are _____

Answer (Please select your correct option)

VuAnswers.com

- 0
- 1
- 2
- 3

correct

Made by: Waqar Siddhu

Question No : 14 of 52

Marks: 1 (Budgeted Time 1 Min)

Determine the values of A , B , C , and D for the sum term $\bar{A} + B + \bar{C} + D$

Answer (Please select your correct option)

VuAnswers.com

- $A = 1, B = 0, C = 0, D = 0$
- $A = 1, B = 0, C = 1, D = 0$
- $A = 0, B = 1, C = 0, D = 1$
- $A = 1, B = 0, C = 1, D = 1$

correct

Made by: Waqar Siddhu

Question No : 15 of 52

Marks: 1 (Budgeted Time 1 Min)

Determine the values of A , B , C , and D for the product term $\bar{A}B\bar{C}D$

Answer (Please select your correct option)

VuAnswers.com

- $A = 0, B = 1, C = 0, D = 1$
- $A = 1, B = 0, C = 1, D = 0$
- $A = 1, B = 1, C = 1, D = 1$
- $A = 0, B = 0, C = 1, D = 0$

correct

Made by: Waqar Siddhu

For More Visit **VU Answer**

Question No : 16 of 52

Marks: 1 (Budgeted Time 1 Min)

A transparent mode means _____

Answer (Please select your correct option)

VuAnswers.com

- Input Hold time is zero (no need to maintain input after clock transition)
- The changes in the data at the inputs of the latch are seen at the output
- The changes in the data at the inputs of the latch are not seen at the output
- Propagation Delay is zero (Output is immediately changed when clock signal is applied)

correct

Made by: Waqar Siddhu

Question No : 17 of 52

Marks: 1 (Budgeted Time 1 Min)

The design and implementation of synchronous counters start from _____

Answer (Please select your correct option)

VuAnswers.com

- Truth table
- K-map
- State table
- State diagram

correct

Made by: Waqar Siddhu

Question No : 18 of 52

Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit whose output depends on the current state and the input is known as _____

Answer (Please select your correct option)

VuAnswers.com

- Moore Machine
- Mealy Machine
- Counter
- Flip Flop

correct

Made by: Waqar Siddhu

For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 19 of 52

Marks: 1 (Budgeted Time 1 Min)

The best state assignment tends to _____.

Answer (Please select your correct option)

VuAnswers.com

- Maximizes the number of state variables that don't change in a group of related states
- Minimizes the number of state variables that don't change in a group of related states
- Minimizes the equivalent states
- Maximizes the equivalent states

correct

Made by: Waqar Siddhu

Question No : 20 of 52

Marks: 1 (Budgeted Time 1 Min)

In _____, the Q output of the last flip-flop of the shift register is connected to the data input of the first flip-flop of the shift register.

Answer (Please select your correct option)

VuAnswers.com

- Moore machine
- Mealy machine
- Johnson counter
- Ring counter

correct

Made by: Waqar Siddhu

Question No : 21 of 52

Marks: 1 (Budgeted Time 1 Min)

Invalid state of NOR based SR latch occurs when _____.

Answer (Please select your correct option)

VuAnswers.com

- S=0, R=0
- S=0, R=1
- S=1, R=0
- S=1, R=1

correct

Made by: Waqar Siddhu

For More Visit **VU Answer**

Question No : 22 of 52 Marks: 1 (Budgeted Time 1 Min)

The operation of J-K flip-flop is similar to that of the SR flip-flop except that the J-K flip-flop _____

Answer (Please select your correct option)

VuAnswers.com

Doesn't have an invalid state

correct

Sets to clear when both $J = 0$ and $K = 0$

It does not show transition on change in pulse

It does not accept asynchronous inputs

Made by: Waqar Siddhu

Question No : 23 of 52 Marks: 1 (Budgeted Time 1 Min)

Following is the circuit diagram of mono-stable device. Which gate will be replaced by the red colored rectangle in the circuit?



Answer (Please select your correct option)

VuAnswers.com

AND

correct

XNOR

NAND

NOR

Made by: Waqar Siddhu

Question No : 24 of 52 Marks: 1 (Budgeted Time 1 Min)

A flip-flop is connected to +5 volts and it draws 5 mA of current during its operation, the power dissipation of the flip-flop is _____

Answer (Please select your correct option)

VuAnswers.com

10 mW

correct

25 mW

64 mW

84 mW

Made by: Waqar Siddhu

Question No : 25 of 52 Marks: 1 (Budgeted Time 1 Min)

RCO Stands for _____

Answer (Please select your correct option) **VuAnswers.com**

- Reconfiguration Counter Output
 - Reconfiguration Clock Output
 - Ripple Counter Output
 - Ripple Clock Output
- correct** *Made by: Waqar Siddhu*

Question No : 26 of 52 Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit, whose output is determined by the current state only is known as _____.

Answer (Please select your correct option) **VuAnswers.com**

- Moore Machine
 - Mealy Machine
 - Counter
 - Flip Flop
- correct** *Made by: Waqar Siddhu*

Question No : 27 of 52 Marks: 1 (Budgeted Time 1 Min)


In asynchronous transmission when the transmission line is idle, _____.

Answer (Please select your correct option) **VuAnswers.com**

- It is set to logic low
 - It is set to logic high
 - Remains in previous state
 - State of transmission line is not used to start transmission
- correct** *Made by: Waqar Siddhu*

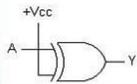Question No : 28 of 52 Marks: 1 (Budgeted Time 1 Min)


The output of this circuit is always _____.



Answer (Please select your correct option) **VuAnswers.com**

- 1
 - 0
 - A correct
 - \bar{A}
- Made by: Waqar Siddhu**

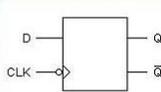Question No : 29 of 52 Marks: 1 (Budgeted Time 1 Min)



Which of the following statement is true regarding above block diagram ?

Answer (Please select your correct option) **VuAnswers.com**

- Triggering takes place on the negative-going edge of the CLK pulse
 - Triggering takes place on the positive-going edge of the CLK pulse correct
 - Triggering can take place anytime during the LOW level of the CLK waveform
 - Triggering can take place anytime during the LOW level of the CLK waveform
- Made by: Waqar Siddhu**

Question No : 30 of 52 Marks: 1 (Budgeted Time 1 Min)

Which is not characteristic of a shift register?

Answer (Please select your correct option) **VuAnswers.com**

- Serial in/parallel in correct
 - Serial in/parallel out
 - Parallel in/serial out
 - Parallel in/parallel out
- Made by: Waqar Siddhu**

For More Visit **VU Answer**

Question No : 31 of 52

Marks: 1 (Budgeted Time 1 Min)

A bidirectional 4-bit shift register is storing the nibble 1110. Its RIGHT/LEFT input is LOW. The nibble 0111 is waiting to be entered on the serial data-input line. After two clock pulses, the shift register is storing _____.

Answer (Please select your correct option)

VuAnswers.com

- 1110
- 0111
- 1000
- 1001

correct

Made by: Waqar Siddhu

Question No : 32 of 52

Marks: 1 (Budgeted Time 1 Min)

Smallest unit of binary data is a _____

Answer (Please select your correct option)

VuAnswers.com

- Bit
- Nibble
- Byte
- Word

correct

Made by: Waqar Siddhu

Question No : 33 of 52

Marks: 1 (Budgeted Time 1 Min)

The high density FLASH memory cell is implemented using _____

Answer (Please select your correct option)

VuAnswers.com

- 1 floating-gate MOS transistor
- 2 floating-gate MOS transistors
- 4 floating-gate MOS transistors
- 6 floating-gate MOS transistors

correct

Made by: Waqar Siddhu

For More Visit **VU Answer**

Question No : 34 of 52 Marks: 1 (Budgeted Time 1 Min)

FIFO is an acronym for _____

Answer (Please select your correct option)

VuAnswers.com

First In, First Out

correct

Fly in, Fly Out

Fast in, Fast Out

None of given options

Made by: Waqar Siddhu

Question No : 35 of 52 Marks: 1 (Budgeted Time 1 Min)

In order to synchronize two devices that consume and produce data at different rates, we can use _____

Answer (Please select your correct option)

VuAnswers.com

Read Only Memory

First In First Out Memory

correct

Flash Memory

Fast Page Access Mode Memory

Made by: Waqar Siddhu

Question No : 36 of 52 Marks: 1 (Budgeted Time 1 Min)

Stack is a _____

Answer (Please select your correct option)

VuAnswers.com

Bust Flash Memory

FIFO memory

LIFO memory

correct

Flash Memory

Made by: Waqar Siddhu

Question No : 37 of 52 Marks: 1 (Budgeted Time 1 Min)

The voltage gain of the Inverting Amplifier is given by the relation _____

Answer (Please select your correct option) **VuAnswers.com**

- $V_{out} / V_{in} = - R_f / R_i$ correct
 - $V_{out} / R_f = - V_{in} / R_i$
 - $R_f / V_{in} = - R_i / V_{out}$
 - $R_f / V_{in} = R_i / V_{out}$
- Made by: Waqar Siddhu**

Question No : 38 of 52 Marks: 1 (Budgeted Time 1 Min)

The process of converting the analogue signal into a digital representation (code) is known as _____

Answer (Please select your correct option) **VuAnswers.com**

- Strobing
 - Amplification
 - Quantization correct
 - Digitization
- Made by: Waqar Siddhu**

Question No : 39 of 52 Marks: 1 (Budgeted Time 1 Min)

A hold action occurs :

Answer (Please select your correct option) **VuAnswers.com**

- After the analog-to-digital conversion
 - During each sample
 - Immediately after a sample correct
 - Before each sample
- Made by: Waqar Siddhu**

For More Visit **VU Answer**

Question No : 40 of 52 Marks: 1 (Budgeted Time 1 Min)

According to the sampling theorem, the sampling frequency should be :

Answer (Please select your correct option)

VuAnswers.com

- Greater than the lowest signal frequency
- Less than half the lowest signal frequency
- Greater than twice the highest signal frequency
- Less than half the highest signal frequency

correct

Made by: Waqar Siddhu

Question No : 41 of 52 Marks: 2 (Budgeted Time 4 Min)

What is the basic function of a comparator?

Answer (Please click here to Add Answer)

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 42 of 52 Marks: 2 (Budgeted Time 4 Min)

What is meant by state assignment process?

Answer (Please click here to Add Answer)

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 43 of 52

Marks: 2 (Budgeted Time 4 Min)

On the fifth clock pulse, a 4-bit Johnson sequence is $Q_0 = 0$, $Q_1 = 1$, $Q_2 = 1$, and $Q_3 = 1$. What will be the sequence after sixth clock pulse? (Assume Q_3 represents the least significant bit)

Answer (Please [click here](#) to Add Answer)

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 44 of 52

Marks: 2 (Budgeted Time 4 Min)

What is meant by Monotonicity of Digital-to-Analog converters?

Answer (Please [click here](#) to Add Answer)

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 45 of 52

Marks: 3 (Budgeted Time 6 Min)

Convert each of the following decimal numbers to Excess-3 codes:
a) 13 b) 43

Answer (Please [click here](#) to Add Answer)

VuAnswers.com

Normal Arial 12 B I U

13=01000110

43=01110110

Made by: Waqar Siddhu

For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 46 of 52

Marks: 3 (Budgeted Time 6 Min)

How can we calculate the frequency of an unknown signal?

VuAnswers.com

Normal Arial 12 B I U

The frequency of the unknown signal can be calculated by counting the number of clock pulses of the unknown signal and dividing the count number by the time interval in which the clock pulses are counted,

Made by: Waqar Siddhu

Question No : 47 of 52

Marks: 3 (Budgeted Time 6 Min)

Write down three characteristics of serial in / serial out 4-bit left shift register.

VuAnswers.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 48 of 52

Marks: 3 (Budgeted Time 6 Min)

How DRAMs are different from SRAMs? Write three point of differences.

VuAnswers.com

Normal Arial 12 B I U

1. SRAM is static while DRAM is dynamic
2. SRAM is faster compared to DRAM
3. SRAM consumes less power than DRAM
4. SRAM uses more transistors per bit of memory compared to DRAM
5. SRAM is more expensive than DRAM
6. Cheaper DRAM is used in main memory while SRAM

Made by: Waqar Siddhu

For More Visit **VU Answer**

For More Visit **VU Answer**

Question No : 49 of 52 Marks: 5 (Budgeted Time 10 Min)

Draw the function table of Full adder circuit.

VuAnswers.com

Answer (Please [click here](#) to Add Answer)

Made by: Waqar Siddhu

Question No : 50 of 52 Marks: 5 (Budgeted Time 10 Min)

Consider a state sequence a, f, d, e, a, b, c, f, d, c. Starting from initial state "a", draw a table for the inputs and outputs for the state diagram given below.

```
graph LR; a((a)) -- "0/0" --> a; a -- "1/0" --> b((b)); b -- "0/1" --> b;
```

VuAnswers.com

Answer (Please [click here](#) to Add Answer)


Made by: Waqar Siddhu

For More Visit **VU Answer**

For More Visit **VU Answer**

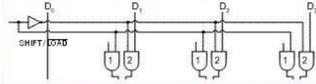Question No : 51 of 52 Marks: 5 (Budgeted Time 10 Min)

Given below is an incomplete circuit diagram of parallel in / serial out shift register, in which Q0, Q1, Q2, Q3, and Clock input are disconnected. Connect above mentioned connections in such a way that functionality of the given circuit is not affected.



Answer (Please [click here](#) to Add Answer) **VuAnswers.com**

Rich text editor toolbar with options: Normal, Arial, 12, B, I, U, and a 100% zoom level. The editor area is empty.

Made by: Waqar Siddhu

Question No : 52 of 52 Marks: 5 (Budgeted Time 10 Min)

Memory chips can be connected together in different manners to increase the total size of the memory. Draw block diagram of 4K x word memory if you are given four 4K x bytes chips.

Empty text area for drawing a block diagram.

Answer (Please [click here](#) to Add Answer) **VuAnswers.com**

Rich text editor toolbar with options: Normal, Arial, 12, B, I, U, and a 100% zoom level. The editor area is empty.

Made by: Waqar Siddhu

For More Visit **VU Answer**